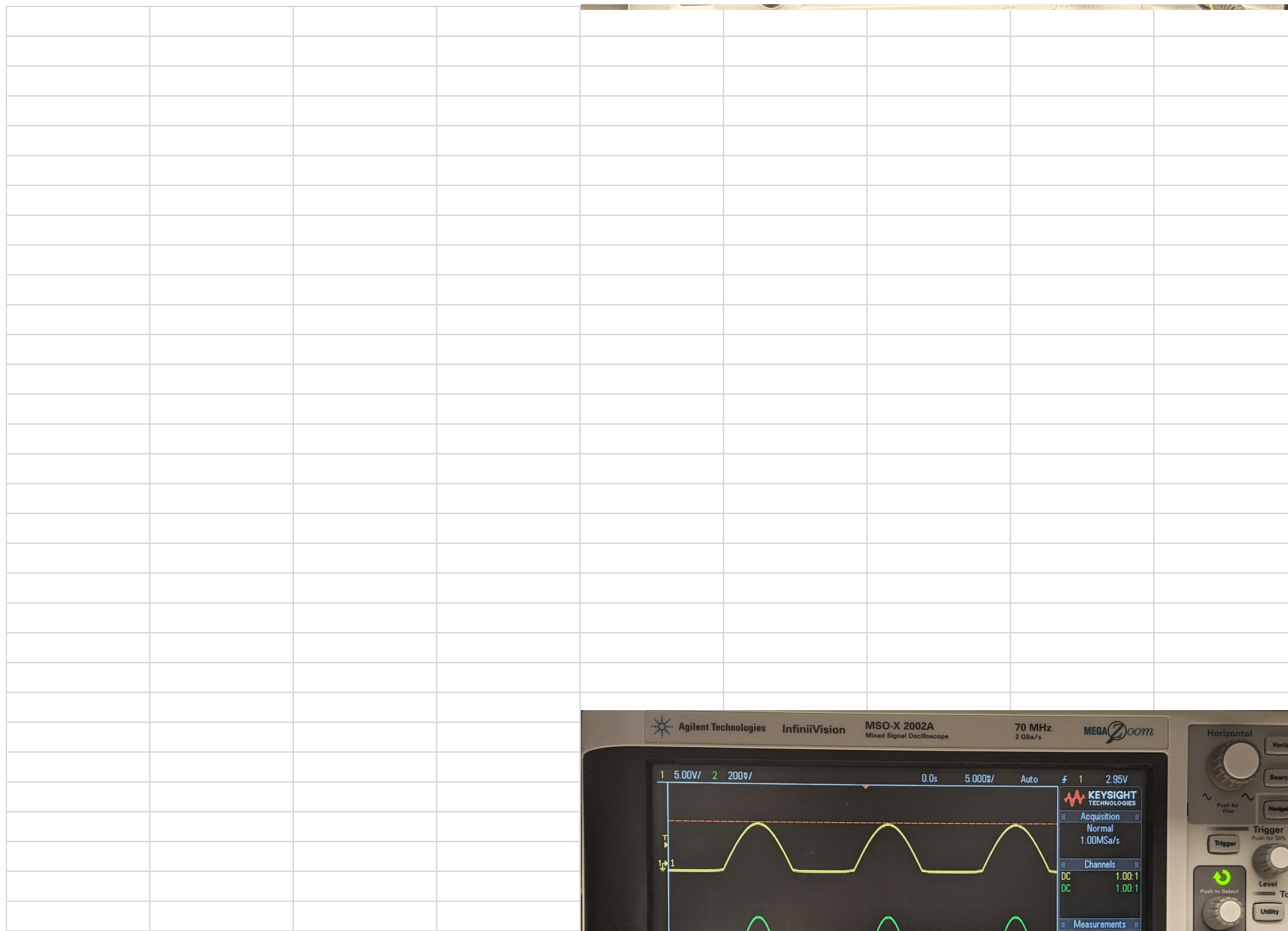


[illegible]





Avg frequency of full wave rectifyer:

60Hz

Average Voltage of full wave rectifyer:

0.0105 V

Capacitor discharge time:

0.018 s

V/time=

0.5833333333

Capactor value:

0.33 F

I

0.1925 A

I\_rs

0.000000206 AAC

Scaling factor

$\sim 10^8$

Current across the load resistor;

0.04044 A

				V_out/R_out				
				0.000003181818				
				Conclusion				
				We learned about full bridge recifiers				